
Name:	Student	#: Si	ignature:	


Time limit: 60 min. Calculators not allowed. All programming questions relate to the NIOS II processor.

1. (2 marks) Use logic gates to design a 2 to 1 multiplexer. Label inputs: **A**, **B**, and **SELECT** and output:

Y?

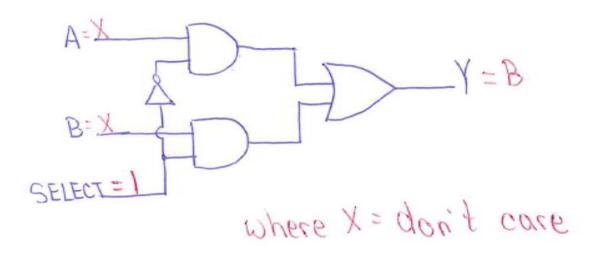

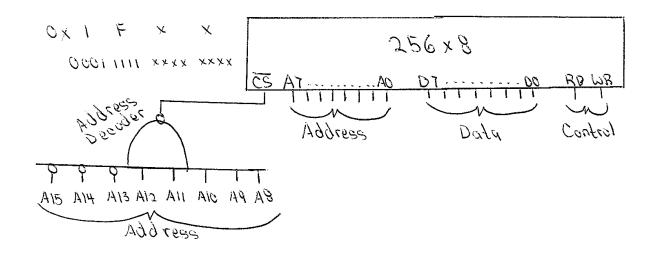2. (5 marks) Draw and label the diagram of a single port 256x8 read write memory chip. Ensure that the memory chip includes an active low chip select line, all address lines, all data lines, a read line and a write line. The memory is to be interfaced to a system with a 16-bit address space (use a NAND gate to perform the address decoding) and this block of memory is to span the address range 0x1F00 to 0x1FFF.



to clear register r6 (set r6 equal to 0x00000000)

d) What is the purpose of the instruction at line 3?

Name: ______ Student #: _____ Signature: _____

7. (5 marks) In each of the separate C-language code segments below, give the final value of a.

	_
unsigned int a=1, b=2;	
if(!b) a++;	a = 1
unsigned int a=4, b=2;	
while(b) b = 3;	a = 4
a = 0;	
unsigned int a=3, *b;	
b = &a	a = 0
*b = 0;	
unsigned int a;	
a = 5;	$a = 0x15 = 21_{10}$
a = a 0x0010;	
unsigned int a=3, b=8;	
while(b){b = b>>1; a++;}	a = 7

Name:	Student #:	Si	ignature:	

- 8. (5 marks) Draw a timing diagram showing the signals (CS, WRITE, READ, d1, and d0) as the following sequence of events occurs:
 - Assume both LEDs are off to start and all five signals are zero
 - LED1 is turned on while LED0 is turned off
 - The data bus (d1 and d0) is used to communicate data to other components not shown
 - LED0 is turned on while LED1 is turned off
 - Both LEDs are turned off
 - At end of timing diagram the state of both LEDs is put onto the data bus

