


Name: Solutions Student #: _____ Signature: _____

Calculators not allowed


1. (4 marks) Complete the table below by converting each of the supplied 8-bit numbers to the base shown.

Value	Binary	Octal	Decimal	Hexadecimal
10011011_2	10011011_2	233_8	155_{10}	$9B_{16}$
357_8	11101111_2	357_8	239_{10}	EF_{16}
255_{10}	11111111_2	377_8	255_{10}	FF_{16}
$8F_{16}$	10001111_2	217_8	143_{10}	$8F_{16}$

 2. (1 mark) Draw a logic gate that uses the input signal: **CONTROL** to determine if the input signal: **INPUT** is allowed to pass to the output signal: **OUTPUT**. When **CONTROL** is low **OUTPUT = INPUT**, when **CONTROL** is high **OUTPUT = 1**. Label all inputs and outputs.



 
3. (2 marks) Use logic gates to design a 2 to 1 multiplexer. Label inputs: **A**, **B**, and **SELECT** and output: **Y**?



4. (1 mark) Label the logic levels (**1** or **0**) on the inputs of the multiplexer in question 3, such that the output **Y = B**. **SOLUTION SHOWN IN RED ABOVE.**

Name: Solutions Student #: _____ Signature: _____

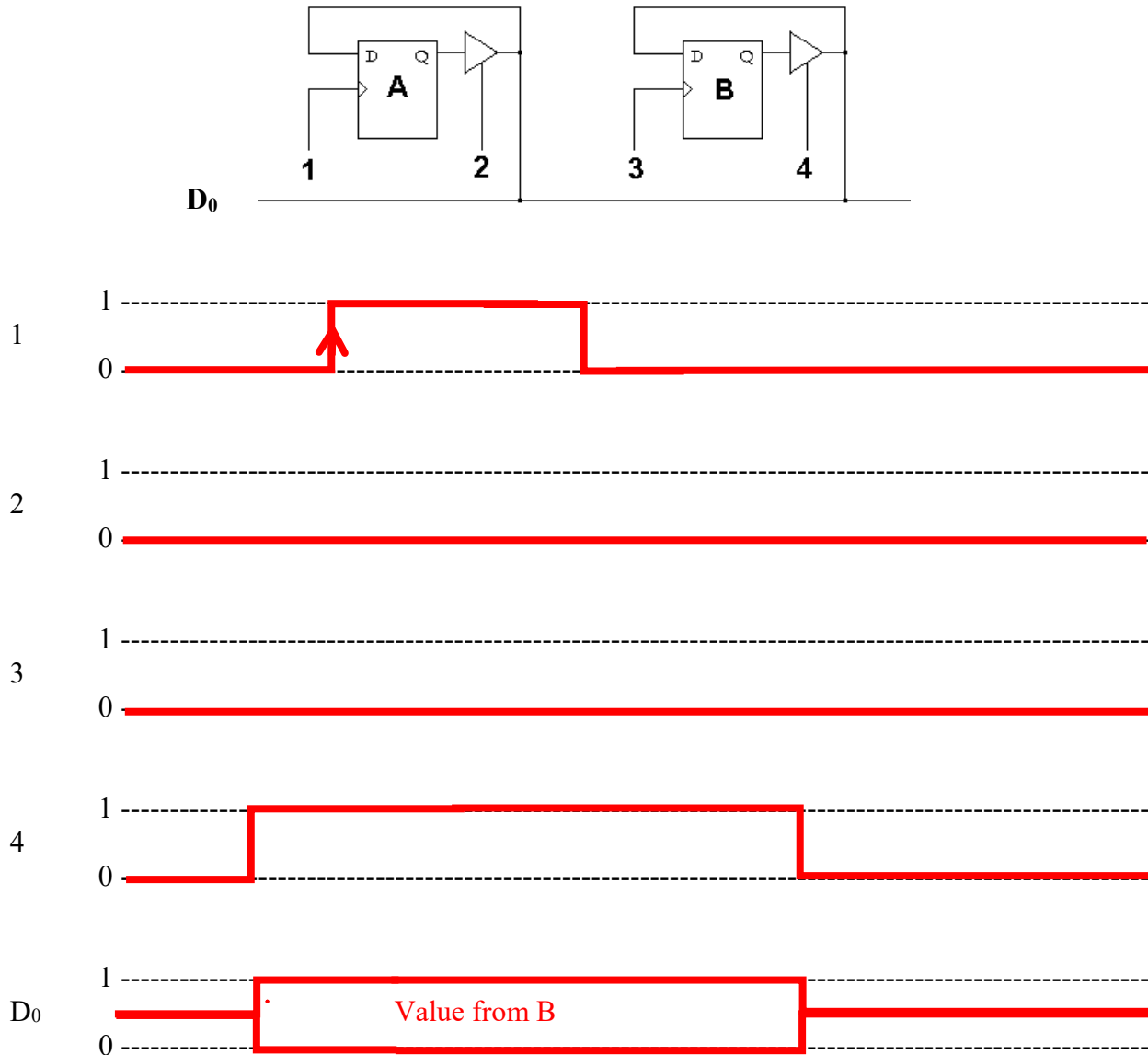5. (5 marks) Draw a timing diagram showing the signals (1,2,3,4) as the value in **B** is copied to **A**. Assume all four signals levels are zero before and after the above operation.



A high on signal 4 places the value from B onto the data bus (READ). While the data is still on the data bus, a rising edge on signal 1 clocks the data from the data bus into A (WRITE). After the rising edge has occurred and the data from B is successfully copied to A, signal 1 can return to low to get ready for the next register A write signal. Signal 4 can also return to low thus returning the data bus to a high impedance state and allowing other devices to use the data bus.